

CSE - 250

Simulation

Project

Name: Mehedi Hasan Shaked

ID: 21301436

Section: 06

Semester: Spring '23

Methodology 1:

- Sum the student ID, to find the value of τ .
- Using that we will find the equivalent resistance of the circuit.
- From there we will find R_1, R_2, R_3 .
- Then we will draw the circuit in LTspice.

1) a) Student ID = 21301436

$$\text{So, total} = 2+1+3+0+1+4+3+6 = 20 \text{ ms}$$

Given, $C = 2 \mu\text{F}$


$$\therefore 5\tau = 20$$

$$\Rightarrow \tau = 4$$


$$\therefore RC = 4$$

$$\Rightarrow R_{eq} = \frac{4}{2} = 2 \text{ k}\Omega$$

P.T.O

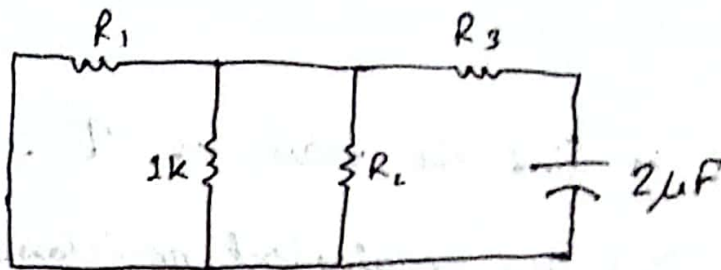

⇓

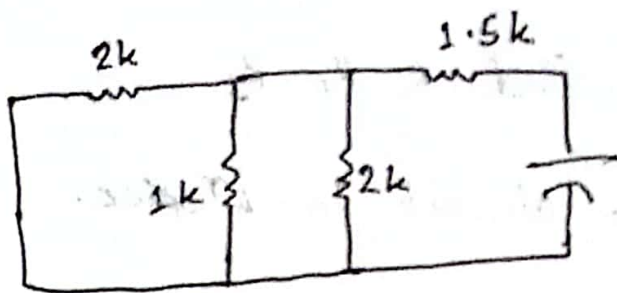


Here, $\left(\frac{1}{2} + \frac{1}{1} + \frac{1}{2}\right)^{-1} + 1.5$

$= 0.5 + 1.5$

$= 2k\Omega$

$= R_{eq.}$

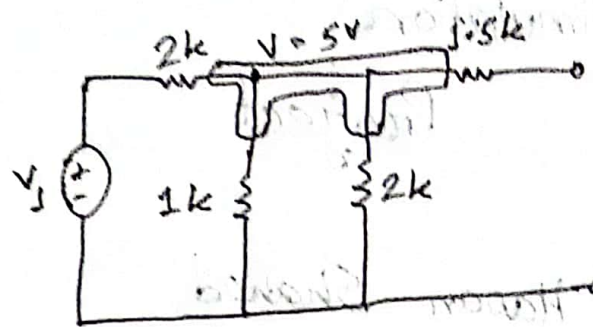b) From the graph we can see the voltage across the capacitor is 5V and -2V.




Here, $V = 5V$ since the resistors are in parallel.

$$\text{So, } \frac{5 - V_1}{2} + \frac{5}{1} + \frac{5}{2} = 0.$$

$$\Rightarrow \frac{5 - V_1 + 10 + 5}{2} = 0$$

$$\Rightarrow V_1 = 20V$$

Again $V = -2V$,

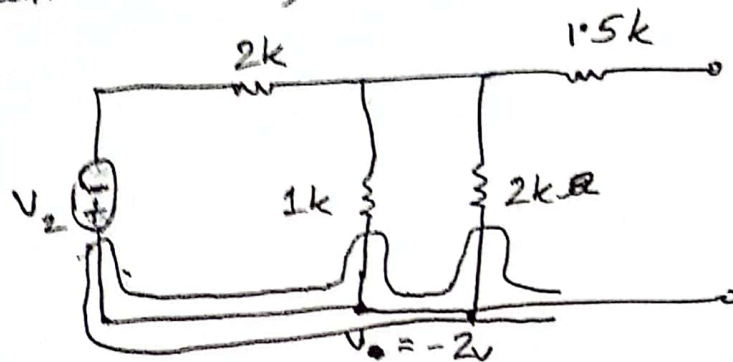


$$\text{Now, } \frac{V_2 + 2}{2} + \frac{2}{1} + \frac{2}{2} = 0$$

$$\Rightarrow \frac{V_2 + 2 + 4 + 2}{2} = 0$$

$$\Rightarrow V_2 = -8V$$

(Ans.)

1)c)

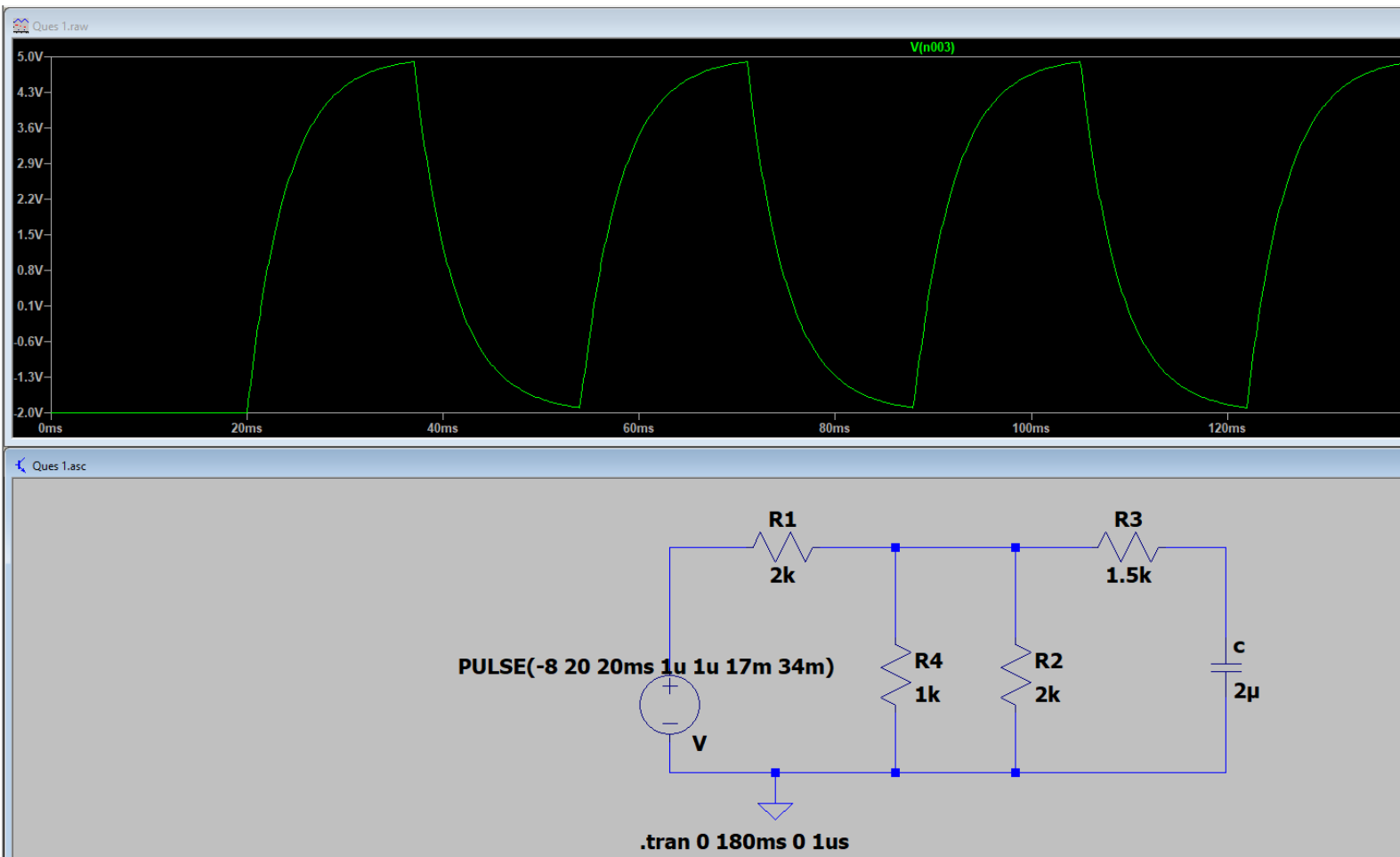


Methodology 2:

- Using the ID we get max power then solving the circuits we get R_{th} which will be R_L value.
- Using LTspice we generate the curve.
- By using mesh we find I_s .
- Then we simulate the original circuit

P.T.O

2) a) total of ID: $2 + 1 + 3 + 0 + 1 + 4 + 3 + 6$

$$= 20 \text{ W}$$

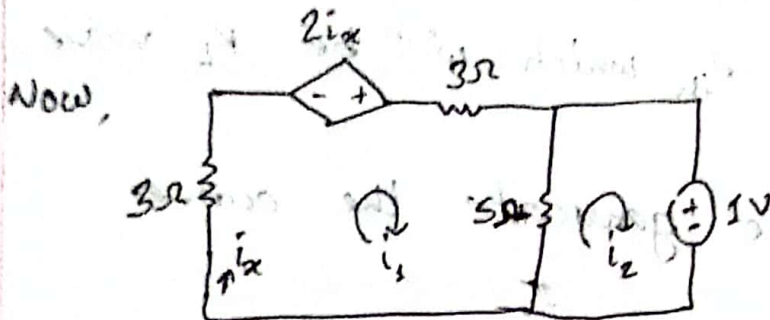

Applying mesh:

$$3i_1 - 2i_1 + 3i_1 + 5i_1 - 5i_2 = 0$$

$$\Rightarrow 9i_1 - 5i_2 = 0$$

$$5i_2 - 5i_1 = 1$$

$$\Rightarrow i_1 = 0.25 \text{ A}$$


$$i_2 = 0.45 \text{ A} = i_o$$


$$\therefore R_{th} = \frac{1}{0.45} = 2.22 \Omega$$

$$\therefore P_{max} = \frac{V_{th}^2}{4R_{th}}$$

$$\Rightarrow V_{th} = 13.326665 \text{ V}$$

2)b)

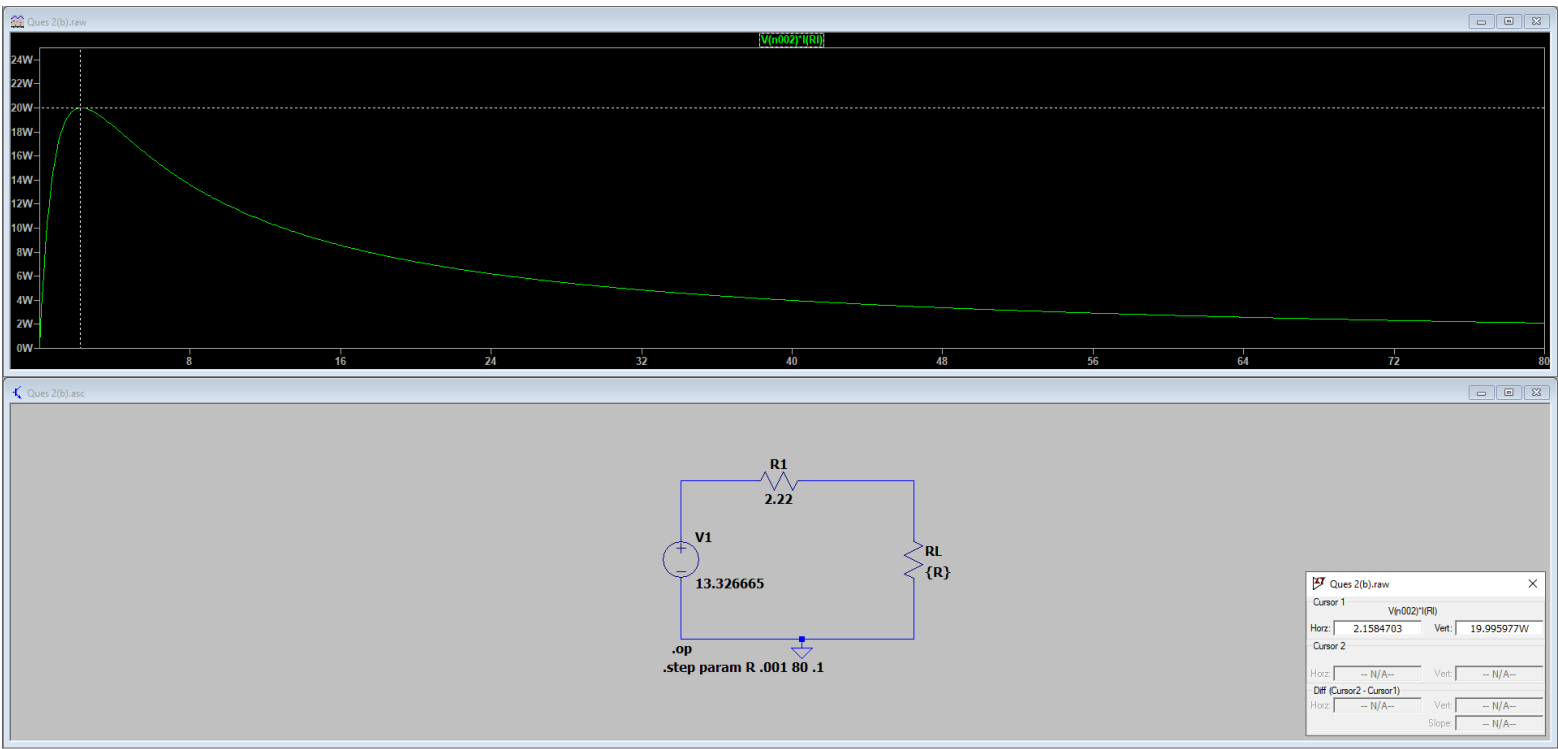

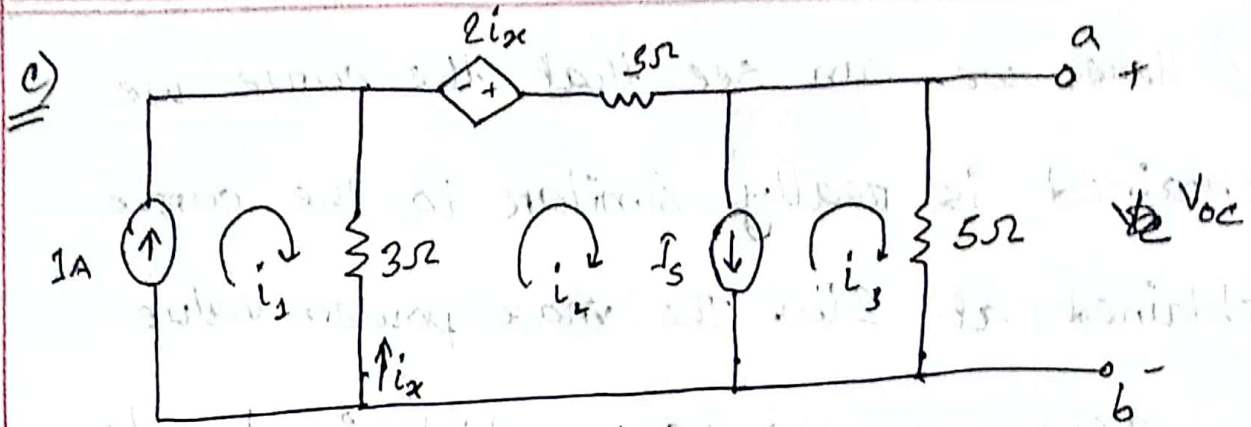

$$i_1 = 1A, \quad i_x = i_2 - i_1, \quad I_s = i_2 - i_3$$

$$= i_2 - 1$$

Applying mesh,

$$3i_2 - 2(i_2 - 1) + 3i_2 + 5i_3 = 0$$

$$3i_2 - 2i_2 + 2 + 3i_2 + 5i_3 = 0$$

$$\Rightarrow 4i_2 + 5i_3 = -2 \quad \text{--- ①}$$


NOW, $i_3 = \frac{V_{oc}}{R}$

$$= \frac{13.326665}{5} = 2.665333 A$$

from eqⁿ ①, $i_2 = -3.082 A$

$$\therefore I_s = -5.747333 A$$

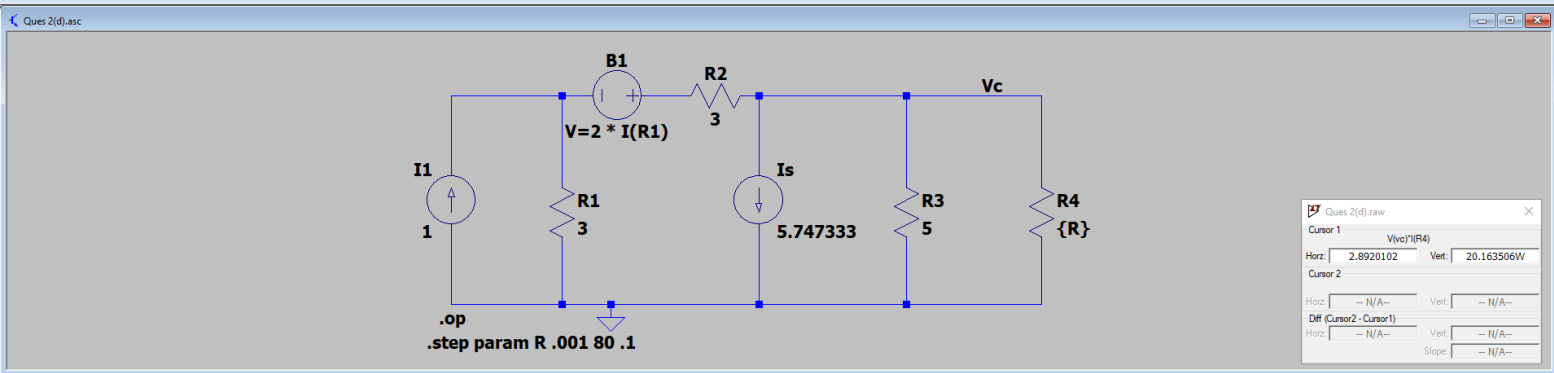d) Here, we can see that the curve we obtained is really similar to the curve obtained at 2(b). The max power value in 2(b) was 10.99 W which is due to the rounding up during the calculation of the thevenin circuit. But in part d we got a pretty accurate answer of 20.16 W. So, the curve derived in part b and d are same.



Ques 2(d).raw

Cursor 1	
Horz	2.8920102
Vert	20.163506W
Cursor 2	
Horz	N/A
Vert	N/A
Diff (Cursor2 - Cursor1)	
Horz	N/A
Vert	N/A
Slope	N/A